

Networks

22. Four wires of equal length and of resistances $10\ \text{ohms}$ each are connected in the form of a square. The equivalent resistance between two opposite corners of the square is

- (a) $10\ \text{ohm}$ (b) $40\ \text{ohm}$
(c) $20\ \text{ohm}$ (d) $10/4\ \text{ohm}$


23. Two resistors are connected (a) in series (b) in parallel. The equivalent resistance in the two cases are $9\ \text{ohm}$ and $2\ \text{ohm}$ respectively. Then the resistances of the component resistors are

- (a) $2\ \text{ohm}$ and $7\ \text{ohm}$ (b) $3\ \text{ohm}$ and $6\ \text{ohm}$
(c) $3\ \text{ohm}$ and $9\ \text{ohm}$ (d) $5\ \text{ohm}$ and $4\ \text{ohm}$

24. Resistors of $1, 2, 3\ \text{ohm}$ are connected in the form of a triangle. If a $1.5\ \text{volt}$ cell of negligible internal resistance is connected across $3\ \text{ohm}$ resistor, the current flowing through this resistance will be

- (a) $0.25\ \text{amp}$ (b) $0.5\ \text{amp}$
(c) $1.0\ \text{amp}$ (d) $1.5\ \text{amp}$

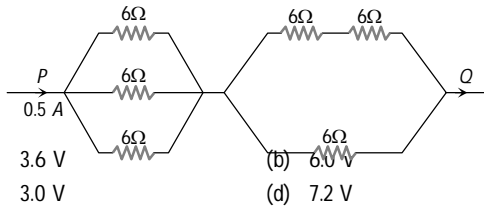
25. Resistances of $6\ \text{ohm}$ each are connected in the manner shown in adjoining figure. With the current $0.5\ \text{ampere}$ as shown in figure, the potential difference $V_P - V_Q$ is



- (a) $3.6\ \text{V}$ (b) $6\ \text{V}$
(c) $3.0\ \text{V}$ (d) $7.2\ \text{V}$


26. The equivalent resistance of the arrangement of resistances shown in adjoining figure between the points A and B is

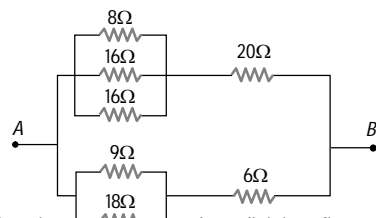- (a) $6\ \text{ohm}$
(b) $8\ \text{ohm}$
(c) $16\ \text{ohm}$
(d) $24\ \text{ohm}$



27. In the network of resistors shown in the adjoining figure, the equivalent resistance between A and B is

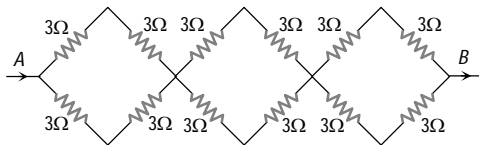- (a) $54\ \text{ohm}$ (b) $18\ \text{ohm}$
(c) $36\ \text{ohm}$ (d) $9\ \text{ohm}$




28. A wire is broken in four equal parts. A packet is formed by keeping the four wires together. The resistance of the packet in comparison to the resistance of the wire will be

- (a) Equal (b) One fourth


- (c) One eighth (d) $\frac{1}{16}\ \text{th}$

29. Four resistances are connected in a circuit in the given figure. The electric current flowing through $4\ \text{ohm}$ and $6\ \text{ohm}$ resistance is respectively

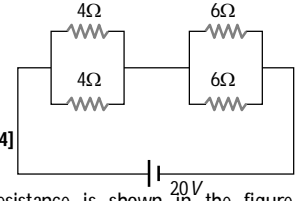- (a) $2\ \text{amp}$ and $4\ \text{amp}$
(b) $1\ \text{amp}$ and $2\ \text{amp}$
(c) $1\ \text{amp}$ and $1\ \text{amp}$ [CPMT 1984]
(d) $2\ \text{amp}$ and $2\ \text{amp}$




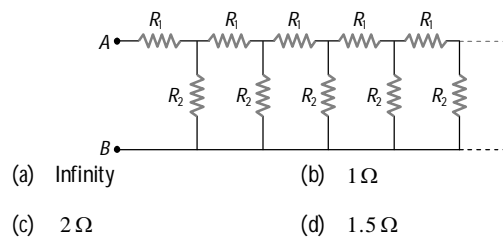30. An infinite sequence of resistance is shown in the figure. The resultant resistance between A and B will be, when $R_1 = 1\ \text{ohm}$ and $R_2 = 2\ \text{ohm}$




- (a) Infinity (b) $1\ \Omega$
(c) $2\ \Omega$ (d) $1.5\ \Omega$

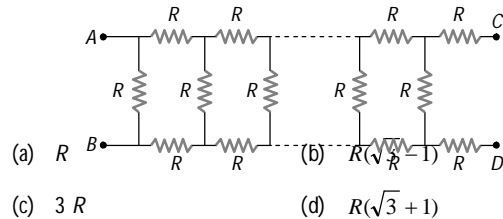31. In the figure, the value of resistors to be connected between C and D so that the resistance of the entire circuit between A and B does not change with the number of elementary sets used is




- (a) R (b) $R(\sqrt{3} - 1)$
(c) $3R$ (d) $R(\sqrt{3} + 1)$

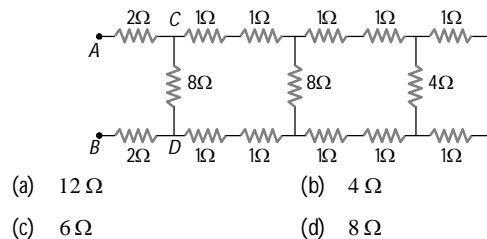32. In the figure shown, the total resistance between A and B is




- (a) $12\ \Omega$ (b) $4\ \Omega$
(c) $6\ \Omega$ (d) $8\ \Omega$

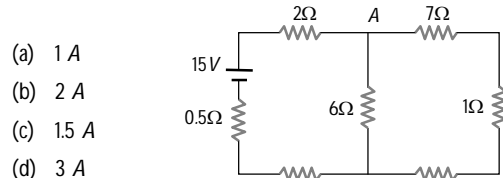33. The current from the battery in circuit diagram shown is



- (a) $1\ \text{A}$
(b) $2\ \text{A}$
(c) $1.5\ \text{A}$
(d) $3\ \text{A}$

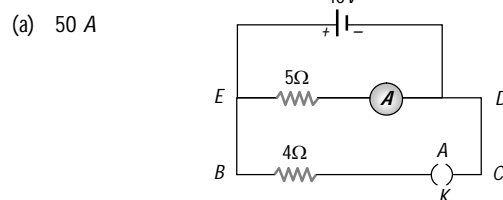34. In the given figure, when key K is opened, the reading of the ammeter A will be




- (a) $50\ \text{A}$

Networks

- (b) $2 A$
 (c) $0.5 A$
 (d) $\frac{10}{9} A$


35. In the given circuit, the potential of the point E is

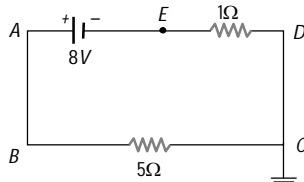- (a) Zero
 (b) $-8 V$
 (c) $-4/3 V$
 (d) $4/3 V$



36. If a resistance R_2 is connected in parallel with the resistance R in the circuit shown, then possible value of current through R and the possible value of R_2 will be

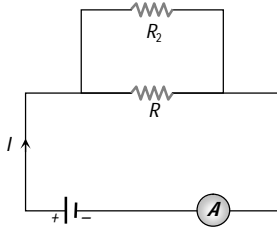- (a) $\frac{I}{3}, R$
 (b) $I, 2R$
 (c) $\frac{I}{3}, 2R$
 (d) $\frac{I}{2}, R$




37. Four wires AB, BC, CD, DA of resistance 4 ohm each and a fifth wire BD of resistance 8 ohm are joined to form a rectangle $ABCD$ of which BD is a diagonal. The effective resistance between the points A and B is

- (a) 24 ohm (b) 16 ohm
 (c) $\frac{4}{3} \text{ ohm}$ (d) $\frac{8}{3} \text{ ohm}$

38. A battery of e.m.f. $10 V$ is connected to resistance as shown in figure. The potential difference $V_A - V_B$ between the points A and B is

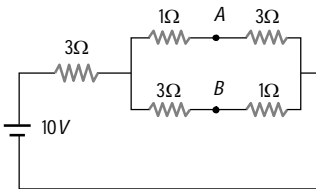- (a) $-2 V$
 (b) $2 V$
 (c) $5 V$
 (d) $\frac{20}{11} V$



39. Three resistances, each of 1 ohm , are joined in parallel. Three such combinations are put in series, then the resultant resistance will be

- (a) 9 ohm (b) 3 ohm
 (c) 1 ohm (d) $\frac{1}{3} \text{ ohm}$

40. A student has 10 resistors of resistance ' r '. The minimum resistance made by him from given resistors is


- (a) $10 r$ (b) $\frac{r}{10}$
 (c) $\frac{r}{100}$ (d) $\frac{r}{5}$

41. Two wires of same metal have the same length but their cross-sections are in the ratio $3:1$. They are joined in series. The

resistance of the thicker wire is 10Ω . The total resistance of the combination will be [CBSE PMT 1995]

- (a) 40Ω (b) $\frac{40}{3} \Omega$
 (c) $\frac{5}{2} \Omega$ (d) 100Ω

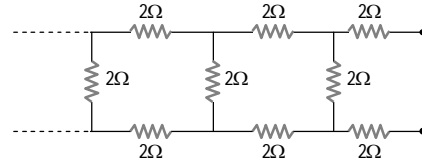
42. The equivalent resistance of the following infinite network of resistances is



- (a) Less than 4Ω
 (b) 4Ω
 (c) More than 4Ω but less than 12Ω
 (d) 12Ω


43. In the figure given below, the current passing through 6Ω resistor is

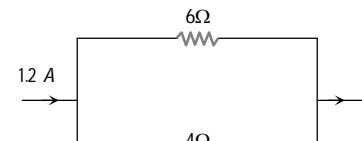- (a) 0.40 ampere
 (b) 0.48 ampere
 (c) 0.72 ampere
 (d) 0.80 ampere




44. Three equal resistances each of value R are joined as shown in the figure. The equivalent resistance between M and N is

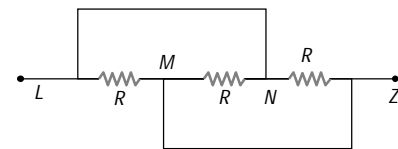- (a) R
 (b) $2R$
 (c) $\frac{R}{2}$
 (d) $\frac{R}{3}$



45. The equivalent resistance between points A and B of an infinite network of resistances each of 1Ω connected as shown, is

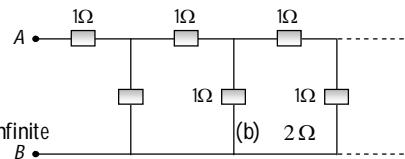- (a) Infinite (b) 2Ω
 (c) $\frac{1 + \sqrt{5}}{2} \Omega$ (d) Zero



46. A copper wire of resistance R is cut into ten parts of equal length. Two pieces each are joined in series and then five such combinations are joined in parallel. The new combination will have a resistance

- (a) R (b) $\frac{R}{4}$
 (c) $\frac{R}{5}$ (d) $\frac{R}{25}$